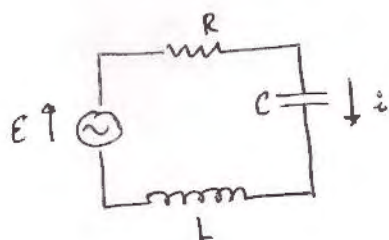


# THE SERIES RLC CIRCUIT

$$\mathcal{E} = \mathcal{E}_m \sin \omega_d t \quad (\text{applied emf})$$





R, L, C in series

$$\rightarrow i = I \sin(\omega_d t - \phi)$$

$\uparrow$  amplitude                       $\uparrow$  phase


## The Current Amplitude

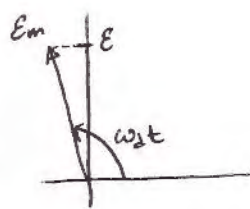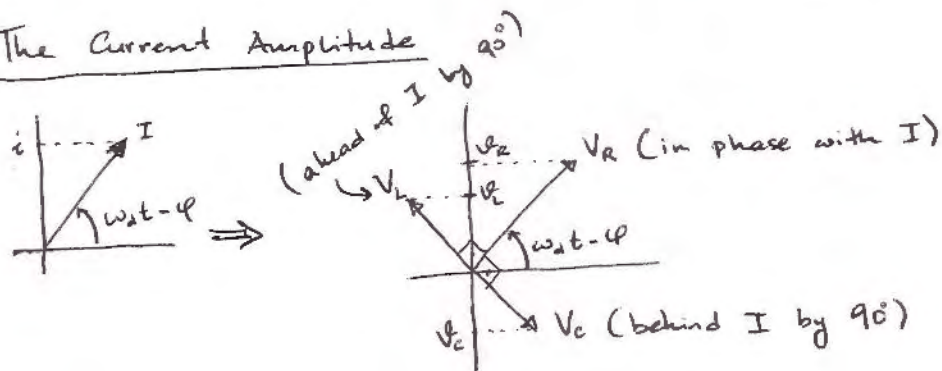

$$\mathcal{E} = V_R + V_C + V_L \quad (\text{at any time})$$

As the phasors rotate together, this equality always holds.

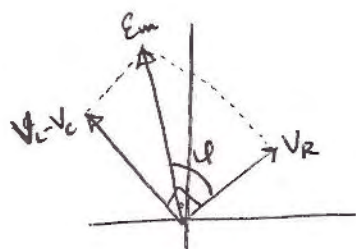$\Rightarrow \mathcal{E}_m$  must be equal to the vector sum of the three voltage phasors  $V_R$ ,  $V_C$  and  $V_L$



$$\begin{aligned} \mathcal{E}_m^2 &= V_R^2 + (V_L - V_C)^2 \\ &= (IR)^2 + (IX_L - IX_C)^2 \end{aligned}$$

$$\Rightarrow I = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}} \rightarrow \text{impedance } Z \text{ of the circuit for the driving angular frequency } \omega_d:$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\Rightarrow I = \frac{\mathcal{E}_m}{Z} \quad X_C = \frac{1}{\omega_d C}, \quad X_L = \omega_d L$$

$$\Rightarrow I = \frac{\mathcal{E}_m}{\sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C}\right)^2}} \quad \left. \begin{array}{l} \text{I depends on the difference between} \\ \omega_d L \text{ and } \frac{1}{\omega_d C} \\ \updownarrow \\ X_L \text{ and } X_C \end{array} \right\}$$

$\rightarrow$  doesn't matter which of the quantities is greater as the difference is squared.

The current we have been describing is the "steady-state" current that occurs after the alternating emf has been applied for some time. When the emf is first applied to a circuit, a brief "transient current" occurs. Its duration (before settling down into the steady state current) is determined by the time constants  $\tau_L = \frac{L}{R}$  and  $\tau_C = RC$  as the inductive and capacitive elements "turn on". The transient current can, for example destroy a motor on start-up if it is not properly taken into account in the motor's circuit design.



### The Phase Constant

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR}$$

$\tan \phi = \frac{X_L - X_C}{R} \rightarrow$  depending on the relative values of the Reactances  $X_L$  and  $X_C$ , it can be one of the three:



- i)  $X_L > X_C$  : The circuit is said to be more inductive than capacitive.  
 $\phi > 0 \rightarrow$  phasor  $I$  rotates behind phasor  $E_m$
- ii)  $X_C > X_L$  : The circuit is said to be more capacitive than inductive.  
 $\phi < 0 \rightarrow I$  rotates ahead of  $E_m$
- iii)  $X_C = X_L$  : The circuit is said to be in Resonance.  
 $\phi = 0$ ,  $E_m$  &  $I$  rotate together in phase.

i)  $\phi > 0$

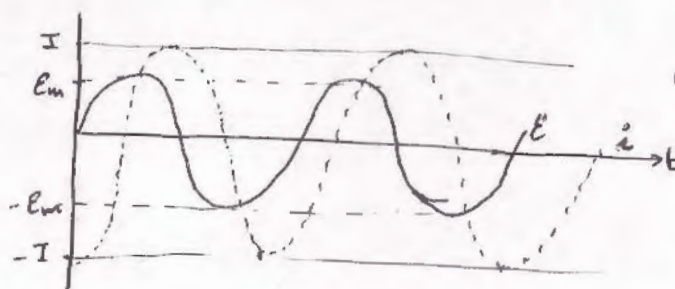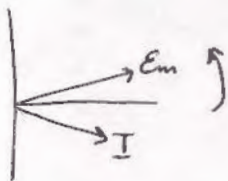



Current lags the emf,  
Curve peaks later.

ii)  $\phi < 0$

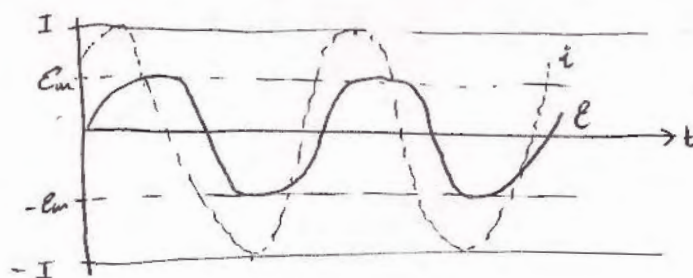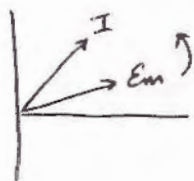

Current leads the emf  
Curve peaks earlier

ii)  $\phi = 0$

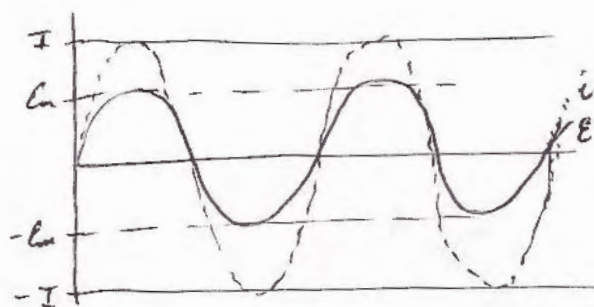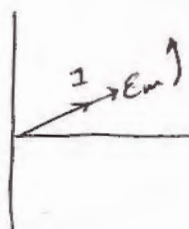

Current and the emf  
are in phase  
They peak together.

## Resonance

$$I = \frac{E_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$
 for a given  $R$ , the amplitude is maximum when  $X_L = X_C$

$$\rightarrow \omega_d L = \frac{1}{\omega_d C} \quad \text{or} \quad \omega_d = \frac{1}{\sqrt{LC}} \quad (\text{maximum } I)$$




Since the natural angular frequency  $\omega$  of the RLC is also equal to  $\frac{1}{\sqrt{LC}}$ , maximum value of  $I$  occurs when the driving angular frequency matches the natural angular frequency,  
 $\rightarrow$  that is at resonance.  $\omega_d = \omega = \frac{1}{\sqrt{LC}}$  (resonance)



**Fig. 31-16** Resonance curves for the driven  $RLC$  circuit of Fig. 31-7 with  $L = 100 \mu\text{H}$ ,  $C = 100 \text{ pF}$ , and three values of  $R$ . The current amplitude  $I$  of the alternating current depends on how close the driving angular frequency  $\omega_d$  is to the natural angular frequency  $\omega$ . The horizontal arrow on each curve measures the curve's *half-width*, which is the width at the half-maximum level and is a measure of the sharpness of the resonance. To the left of  $\omega_d/\omega = 1.00$ , the circuit is mainly capacitive, with  $X_C > X_L$ ; to the right, it is mainly inductive, with  $X_L > X_C$ .

Driving  $\omega_d$  equal to natural  $\omega$

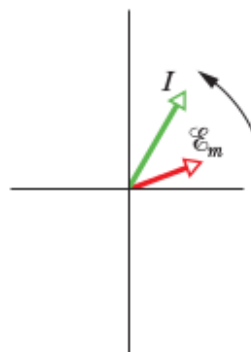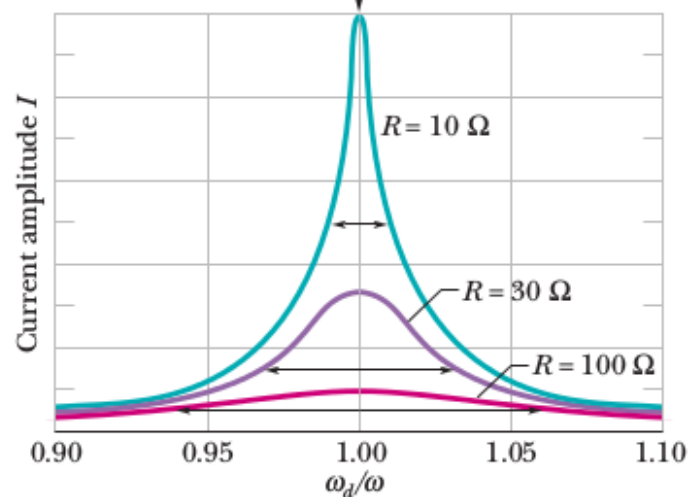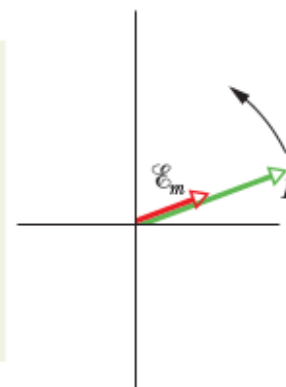- high current amplitude
- circuit is in resonance
- equally capacitive and inductive
- $X_C$  equals  $X_L$
- current and emf in phase
- zero  $\phi$



Low driving  $\omega_d$

- low current amplitude
- ICE side of the curve
- more capacitive
- $X_C$  is greater
- current leads emf
- negative  $\phi$

High driving  $\omega_d$

- low current amplitude
- ELI side of the curve
- more inductive
- $X_L$  is greater
- current lags emf
- positive  $\phi$

