

CIRCUITS

Restriction : DC : Direct Current Circuits
to the course

Pumping the Charges:

Capacitors are OK but very limited.

→ Charge Pump: EMF device EMF: \mathcal{E}

↳ "Electromotive Force" (outdated definition)

Previously (up until now) Electric field produced forces
that moved the charge carriers

the motion of charge carriers in terms of now:

Required Energy

→ an EMF device supplies
the energy for the motion
via the work it exerts.


A common EMF device: BATTERY

Most influences our lives: electric generator

solar cells

fuel cells

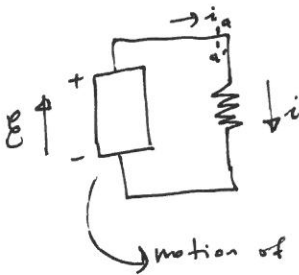also living things (electric eels,
human beings
("matrix"))



motion of positive charge carriers opposite of the \vec{E} field between the
terminals (inside the EMF device)

→ Thus there must be some source of
energy within the device.

Energy Source: Chemical: battery, fuel cell

Mechanical: Electric generator

Also, even temperature differences (thermopiles, sun)

in dt time, dq charge passes through a cross-section $a-a'$

dW to move dq

$$\mathcal{E} = \frac{dW}{dq}$$

Work per unit charge that the device does to move charges from low potential terminal to the high potential terminal

$$[\mathcal{E}] = \frac{J}{C} = \text{Volt}$$

Ideal EMF: The potential difference between the terminals is equal to the emf of the device.


(e.g., a 12V battery always supplies a potential difference of 12V, always)

Real life: The EMF device has an internal Resistance


"but" (When it's not connected)

$$V_{\text{terminals}} = \mathcal{E}$$

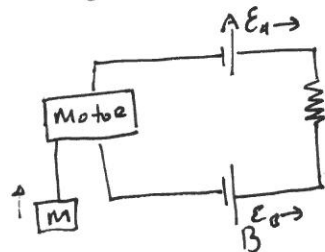When the EMF device is connected, the device transfers energy to the charge carriers passing through it.




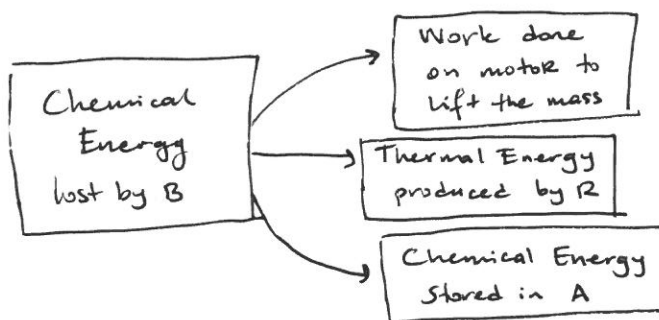$\mathcal{E}_B > \mathcal{E}_A \rightarrow B$ is charging A



Calculating the current in a single-loop circuit

i.) via Energy Conservation:

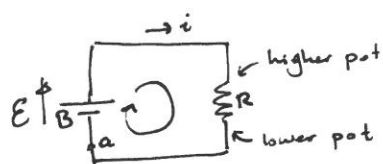

$P = i^2 R \rightarrow$ in a time interval dt , an amount of energy $i^2 R dt$ will appear in the resistor as thermal energy.

$dq = i dt$ will have moved through battery \mathcal{E}

$$dW = \mathcal{E} dq = \mathcal{E} i dt$$

$$\rightarrow \mathcal{E} i dt = i^2 R dt$$

$$\mathcal{E} = iR \rightarrow \boxed{i = \frac{\mathcal{E}}{R}}$$

ii.) via Potential:

The sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero \therefore Kirchhoff's Loop Rule

the potential at a: V_a
①

when we pass the battery, the change in the potential = \mathcal{E}
②

R: $V = iR$: it must decrease since we are moving from higher to lower potential

$$\Rightarrow \underline{\Delta V = -iR} \quad \text{③}$$

$$\Rightarrow V_a + \mathcal{E} - iR = V_a \quad (\text{analogy with heights})$$

① ② ③

$$\rightarrow \mathcal{E} - iR = 0$$

$$\Rightarrow \boxed{i = \frac{\mathcal{E}}{R}}$$


Resistance Rule: For a move through a resistance in a direction same as the current, the change in the potential is: $-iR$
(opposite direction of the current: iR)

EMF Rule: For a move through an ideal emf device in the same direction of the emf arrow, the change in the potential is \mathcal{E}

(for the opposite direction: $-\mathcal{E}$)


Other Single-loop Circuits

Internal Resistance

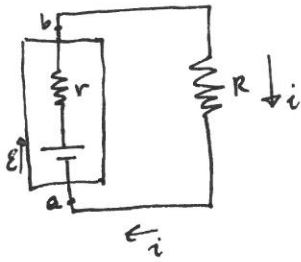


$$\mathcal{E} - ir - iR = 0$$
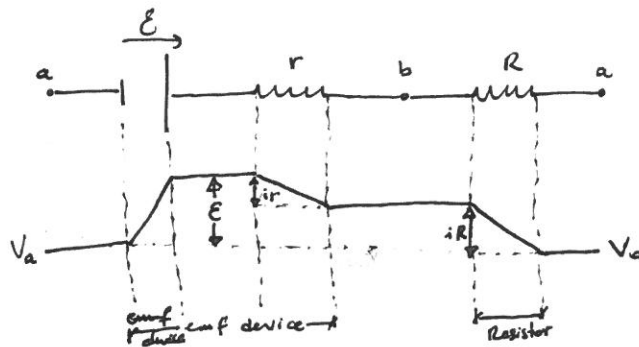
$$i = \frac{\mathcal{E}}{R+r} \quad \left(\rightarrow r \rightarrow 0: i = \frac{\mathcal{E}}{R} \right)$$



Resistances in Series

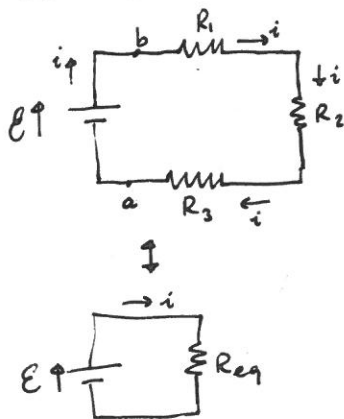

The resistances in series have the identical current i

The Sum of potential differences across the resistances is equal to the applied potential difference of V

Resistances in series can be replaced with an equivalent Resistance R_{eq} that has the same current i and the same total potential difference V as the original resistances.


$$\rightarrow i) \mathcal{E} - iR_1 - iR_2 - iR_3 = 0 \rightarrow i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$

$$ii) \mathcal{E} - iR_{eq} = 0 \rightarrow i = \frac{\mathcal{E}}{R_{eq}}$$

$$i + ii : \Rightarrow R_{eq} = R_1 + R_2 + R_3$$

$$(\text{in general}) \quad R_{eq} = \sum_{j=1}^n R_j \quad \underline{\text{Resistances in Series}}$$

Potential Difference Between two points

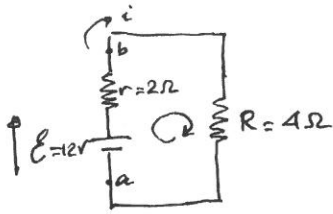

$$V_a + E - ir = V_b$$

$$V_b - V_a = E - ir$$

$$i = \frac{E}{R+r} \rightarrow V_b - V_a = E - \frac{E}{R+r} r = \frac{E}{R+r} R$$

$$V_b - V_a = \frac{12V}{4\Omega + 2\Omega} 4\Omega = 8V$$

Suppose we move counter-clockwise:

$$V_a + iR = V_b$$

$$V_b - V_a = iR = \frac{E}{R+r} R \quad \checkmark$$

* Potential Difference Across a Real Battery


$$V = E - ir$$

$$(E=12V, r=2\Omega, R=4\Omega) \rightarrow E=12V \text{ but } V=8V$$


↳ note that the result depends on the value of the current through the battery.

different circuit \rightarrow different current \Rightarrow different V

* Grounding a circuit

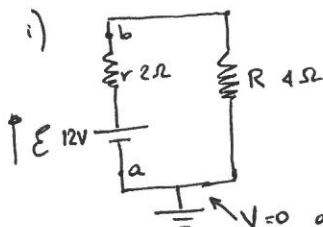
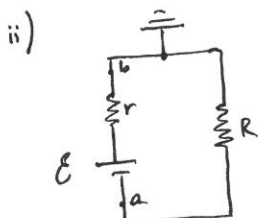
$$V=0 \text{ at the grounding point} \rightarrow V_a=0 \rightarrow V_b=8V$$



$$\rightarrow V_b=0 \rightarrow V_a=-8V$$

In both cases

$$V_b - V_a = 8V$$

Power, Potential and EMF


the net rate
of energy
transfer from
the emf device
to charge
carriers

$$P = iV, \quad V = \mathcal{E} - ir \Rightarrow P = i(\mathcal{E} - ir) = i\mathcal{E} - i^2r$$

$$P_r = i^2r \quad (\text{internal dissipation rate})$$

$$\Rightarrow P_{\text{emf}} = i\mathcal{E} \quad (\text{power of emf device})$$

Example

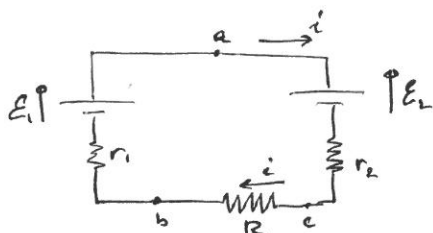

$$\mathcal{E}_1 = 4.4\text{V} \quad \mathcal{E}_2 = 2.1\text{V}$$

$$r_1 = 2.3\Omega \quad r_2 = 1.8\Omega \quad R = 5.5\Omega$$

a.) Current in the circuit?

$$\text{a.} \quad -\mathcal{E}_1 + ir_1 + iR + \mathcal{E}_2 = 0$$

$$\rightarrow i = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R + r_1 + r_2} = \dots = 0.2396\text{A} \approx 240\text{mA}$$


b.) Potential Diff between the terminals of Battery 1?

$$\text{b.} \quad V_b - ir_1 + \mathcal{E}_1 = V_a$$

$$V_a - V_b = -ir_1 + \mathcal{E}_1 = \dots = 3.84\text{V} \approx 3.8\text{V} > 0$$

↓
less than
the emf of the battery.

Example

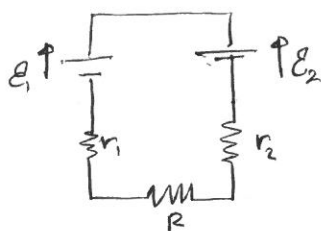

a.) What value must R have

if the current in the circuit is 1mA?

$$\mathcal{E}_1 = 2\text{V}, \quad \mathcal{E}_2 = 3\text{V}, \quad r_1 = r_2 = 3\Omega$$




$$i = \frac{\mathcal{E}_2 - \mathcal{E}_1}{r_1 + r_2 + R} \rightarrow R = \frac{\mathcal{E}_2 - \mathcal{E}_1}{i} - r_1 - r_2 = \dots = 9.9 \times 10^2 \Omega$$

b.) What is the rate at which thermal energy appears in R?

$$P = i^2R = \dots = 9.9 \times 10^{-4}\text{W}$$

Example

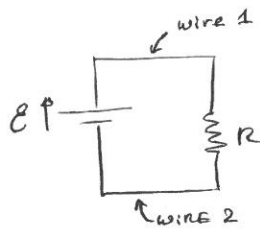

$$R = 6 \Omega$$

$$\mathcal{E} = 12 \text{ V (ideal)}$$

$$l_{\text{wires}} = 20 \text{ cm}$$

$$r_{\text{wires}} = 1 \text{ mm}$$

$$\text{Copper wires } (\rho = 1.69 \times 10^{-8} \Omega \cdot \text{m})$$

a.) $V_R = ?$

$$R_{\text{wire}} = \rho \frac{L}{A} = \rho \frac{L}{\pi r^2} = \dots = 0.0011 \Omega$$

$$R_{\text{tot}} = 2 R_{\text{wire}} + R = 6.0022 \Omega$$

$$i = \frac{\mathcal{E}}{R_{\text{tot}}} = \dots = 1.9993 \text{ A}$$

$$R = 6 \Omega \rightarrow V = iR = \dots = 11.996 \text{ V} \approx 12 \text{ V}$$

b.) Each of the two sections of the wire?

$$V_{\text{wire}} = i R_{\text{wire}} = \dots = 2.15 \text{ mV}$$


c.) Rate of Energy lost to thermal Energy in R?

$$P = i^2 R = 23.98 \text{ W} \approx 24 \text{ W}$$

d.) Rate of energy lost in each section of wire?

$$P = i^2 R_{\text{wire}} = 4.3 \text{ mW}$$

MULTILOOP CIRCUITS

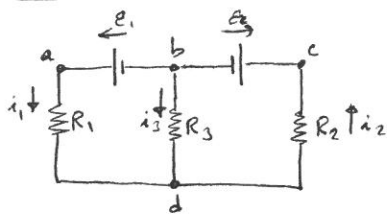

Two junctions: b, d

Three branches: bad, bcd, bd
left right central

$$d: i_1 + i_3 = i_2$$

The sum of currents entering any junction must be equal to the sum of currents leaving that junction.

KIRCHHOFF'S JUNCTION RULE

→ Conservation of charge for a steady flow.


Three loops: $\overset{\text{left}}{\text{badb}}$ $\overset{\text{right}}{\text{bcd b}}$ $\overset{\text{big loop}}{\text{badcb}}$

$$\begin{aligned} \text{Left loop: } E_1 - i_1 R_1 + i_3 R_3 &= 0 \\ \text{Right loop: } -i_3 R_3 - i_2 R_2 - E_2 &= 0 \\ \text{Big loop: } E_1 - i_1 R_1 - i_2 R_2 - E_2 &= 0 \end{aligned}$$

3 eqns, 3 unknowns

$$\begin{pmatrix} 1 & -1 & 1 \\ R_1 & 0 & -R_3 \\ 0 & -R_2 & -R_3 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ E_1 \\ E_2 \end{pmatrix}$$

RESISTANCES IN PARALLEL

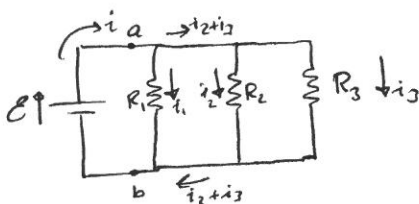

All of the Resistances have the same potential difference V

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}, \quad i_3 = \frac{V}{R_3}$$

$$i = i_1 + i_2 + i_3 = V \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$i = \frac{V}{R_{eq}}$$

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$2R: R_{eq} = \frac{R_1 R_2}{R_1 + R_2} \quad ; \quad \frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j} \quad (n \text{ resistances in parallel})$$

The Voltmeter & Ampermeter


R_A of the ampermeter must be very much smaller.

R_V of the voltmeter must be very much larger.

A, V, $\Omega \rightarrow$ multimeter

RC Circuits

Time Varying Current

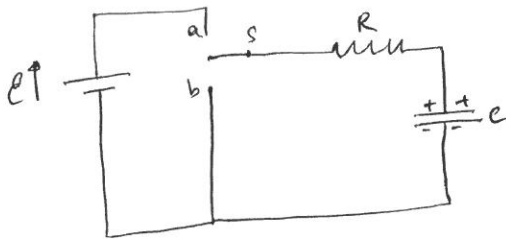

Charging S: a

Discharging S: b

Charging: $\mathcal{E} - iR - \frac{q}{C} = 0$



potential difference across capacitor } negative because the capacitor's top plate is at a higher potential than the lower \rightarrow there is a drop as we move down.


$i = \frac{dq}{dt}$: the charge on the capacitor increases as the current is flowing with time.

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E} \quad (\text{Charging eqn.})$$

$t=0: q=0$ } Solution to the charging eqn.

$$q = C\mathcal{E}(1 - e^{-t/RC}) \quad \text{Charging a capacitor}$$

$t \rightarrow \infty: q = C\mathcal{E}$

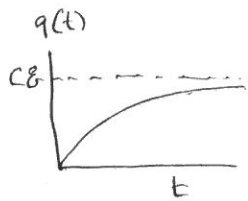


$$i = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-t/RC}$$

$$i_0 = \frac{\mathcal{E}}{R}, \quad i_{t \rightarrow \infty} = 0$$

$$q = CV_c \rightarrow V_c = \frac{q}{C} = \mathcal{E}(1 - e^{-t/RC})$$

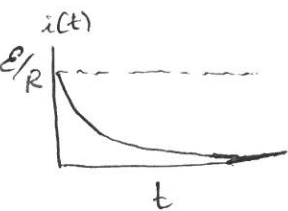$\nearrow t=0: V_c=0$
 $\searrow t \rightarrow \infty: V_c=\mathcal{E}$



The time constant

RC has dimensions of time
↳ Capacitive time constant

$$\tau = RC$$

$$t = \tau = RC: q = CE(1 - e^{-1}) = 0.63CE$$

greater τ , greater charging time

Discharging a capacitor

Switch $S: b$

$$-iR + \frac{q}{C} = 0$$

$i = -\frac{dq}{dt}$ → the charge on the capacitor is decreasing as the current flows in the circuit with time

$$\rightarrow R \frac{dq}{dt} + \frac{q}{C} = 0 \rightarrow q = \underbrace{q_0}_{CV_0} e^{-t/RC}$$

at τ : $q = q_0 e^{-1} = 37\%$ of the initial charge

$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right) e^{-t/RC} \quad (\text{discharging})$$

↓
charge is decreasing

Capacitance Derivation of $q = CE(1 - e^{-t/RC})$

$$R \frac{dq}{dt} + \frac{q}{C} = \mathcal{E}$$

$$\frac{dq}{dt} + \frac{q}{RC} = \frac{\mathcal{E}}{R}$$

$$q = q_p + K e^{-at} \quad a = \frac{1}{RC} \quad t \rightarrow \infty \quad \frac{dq}{dt} = 0 \rightarrow \text{no further current} \quad q = q_p$$

↓
particular solution

$$q_p = CE$$

$$\Rightarrow q = CE + K e^{-at}$$

$$t=0: q=0$$


$$0 = CE + K$$

$$K = -CE$$

$$\Rightarrow q = CE - CE e^{-t/RC}$$

$$q = CE(1 - e^{-t/RC})$$

Example (Quiz)

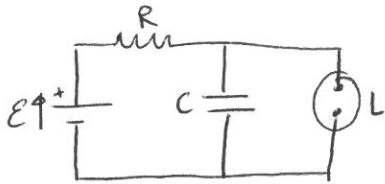

$V_L = 72\text{V}$ Current through the lamp
only when V reaches V_L

$$V = 95\text{V}$$

$$C = 0.15\mu\text{F}$$

In order to have the Lamp
flashes two times per second,
what should the value of R be?

$$V_L = E(1 - e^{-t/RC})$$

$$R = \frac{t^{\leftarrow 0.55}}{C \ln[E/(E - V_L)]} = \dots = 2.35 \times 10^6 \Omega$$

$$\frac{V_L}{E} = 1 - e^{-t/RC}$$

$$1 - \frac{V_L}{E} = e^{-t/RC}$$

$$-t/RC = \ln\left(\frac{E - V_L}{E}\right)$$

$$t/RC = \ln\left(\frac{E}{E - V_L}\right)$$

$$R = \frac{t}{C \ln\left(\frac{E}{E - V_L}\right)}$$

MAGNETIC FIELDS

Magnets \rightarrow Fridge Magnets to CD/DVD, harddisks, speakers, security alarms

What Produces a magnetic field?

electric charge $\rightarrow \vec{E}$

Magnetic charge $\xrightarrow{?} \vec{B}$

\hookrightarrow magnetic monopoles?

How:

- i) Moving charges like a current in a wire \rightarrow electromagnet
- ii) By means of elementary particles such as electrons
 \rightarrow intrinsic magnetic field around them
adds up to make a permanent magnet.

Definition of \vec{B}

$$\vec{E} = \frac{\vec{F}_E}{q} \quad \begin{array}{l} \rightarrow \text{Measured force} \\ \leftarrow \text{test charge } q \end{array}$$

Since we have not yet found a magnetic Monopole, we can't do it like that.

$\rightarrow \vec{F}_B$ exerted on a moving electrically charged test particle.

$$|\vec{F}_B| \propto v \sin \varphi$$

$$\vec{F}_B \perp \vec{v} \Rightarrow B = \frac{F_B}{|q|v}$$

$$\vec{F}_B = q \vec{v} \times \vec{B}$$

$$|\vec{F}_B| = |q| v B \sin \varphi$$

\hookrightarrow angle between \vec{v} and \vec{B}

Finding the Magnetic force on a particle

$$F_B \propto q \& v$$

↓ ↘
 $q=0$ or $v=0 \rightarrow F=0$

$$F=0 \text{ also if } \vec{v} \parallel \vec{B} \quad (\varphi=0^\circ \text{ or } \varphi=180^\circ)$$

$$\text{and } F=F_{\max} \text{ if } \varphi=90^\circ$$

⇒ Right hand Rule: Tip of the fingers point in the \vec{v} direction,
palm is turned in the direction of \vec{B}
→ Thumb points the force due to $\vec{v} \times \vec{B}$
(if $q < 0 \rightarrow$ opposite direction)

\vec{F}_B is always perpendicular to \vec{v} and \vec{B}

→ \vec{F}_B never has a component parallel to \vec{v}
→ \vec{F}_B can not change a particle's speed v
(kinetic energy)
but only the direction of \vec{v} .

$$[B] = \frac{N}{C \cdot m/s} = 1 \text{ Tesla} = 1 T$$

$$1 T = 1 \frac{\text{Newton}}{C/s \cdot m} = 1 \frac{N}{A \cdot m}$$


$$1 T = 10^4 \text{ Gauss} = 10^4 G$$

↳ Earth's surface

Surface of a neutron star	$10^8 T$
Near big electro-magnet	$1.5 T$
Near small electro-magnet	$10^{-2} T$
Earth's surface	$10^{-4} T$
Space	$10^{-10} T$
Smallest value in a magnetically shielded room	$10^{-14} T$

Magnetic Field Lines

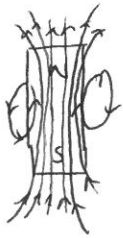- 1) The Direction of the tangent to a magnetic field line at any point gives the direction of \vec{B} at that point.
- 2) Spacing: denser lines \rightarrow stronger \vec{B} .




The lines leave from one end (North pole: N)
and enter from the other (South pole: S)

\rightarrow magnetic dipole
 \downarrow
two poles

Opposite Poles attract each other
Like poles Repel each other

Earth: S

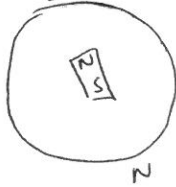

But we already call S as North Pole
so "geomagnetic north pole"

Example: \vec{B} ($=1.2\text{ mT}$) upward

proton K.E. = $K = 5.3\text{ MeV}$ South to north



$$m_p = 1.67 \times 10^{-27} \text{ kg}, \quad F_B = ?$$

$$K = \frac{1}{2} m v^2 \rightarrow v = \sqrt{\frac{2K}{m}} = 3.2 \times 10^9 \text{ m/s}$$

$$F_B = |q| v B \sin \theta \quad \leftarrow 90^\circ \quad = \dots = 6.1 \times 10^{-15} \text{ N}$$

$$a = \frac{F_B}{m} = 3.7 \times 10^{12} \text{ m/s}^2$$

Direction: ?

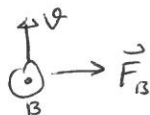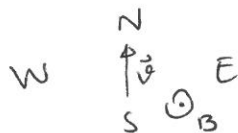

(W \rightarrow E)

if it was an electron:

(E \rightarrow W)

opposite direction.


⊙ Coming towards you
(out of the page)

⊗ moving away from you
(into the page)

CROSSED FIELDS: DISCOVERY OF ELECTRON

if $\vec{E} \neq 0$ & $\vec{B} \neq 0$
& $\vec{E} \perp \vec{B}$ \rightarrow Crossed Fields

1897 J.J. Thomson @ Cambridge University

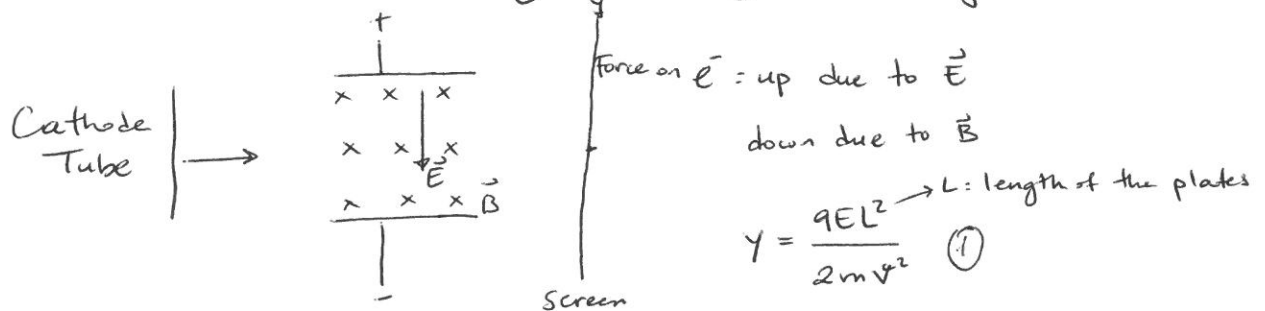

When B and E is adjusted such that they cancel each other:

$$|q|E = |q|vB \sin(90^\circ) = |q|vB$$

$$\Rightarrow v = \frac{E}{B} \quad (2)$$

$$(1) + (2): \quad \boxed{\frac{m}{|q|} = \frac{B^2 L^2}{2YE}}$$

\downarrow
Measurable

$L = vt \rightarrow t = \frac{L}{v}$

$F = qE$


$a = \frac{F}{m} = \frac{qE}{m}$

$y = \frac{1}{2} at^2 = \frac{1}{2} \frac{qE}{m} t^2 = \frac{1}{2} \frac{qE}{m} \frac{L^2}{v^2}$

Derivation of (1):

CROSSED FIELDS: THE HALL EFFECT

1879 Edwin Hall (24 years old)

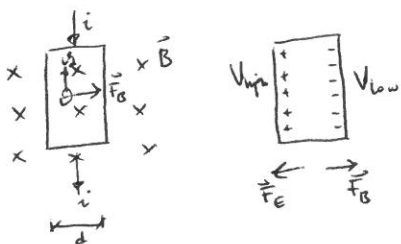

$$V = Ed$$

$$eE = ev_d B$$


$$v_d = \frac{v}{ne} = \frac{i}{neA}$$

$$\rightarrow n = \frac{Bi}{Vde}$$

$$\downarrow$$

$d = \frac{A}{d}$: thickness

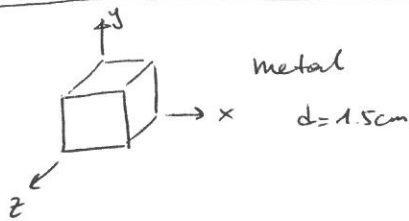Potential Difference Setup Across a moving conductor




moving in positive y direction,
constant $v = 4.0 \text{ m/s}$

$$\vec{B} = 0.05 \hat{k} \text{ T}$$


- a.) Which cube face is at a lower effective potential?
and which is at a higher potential?
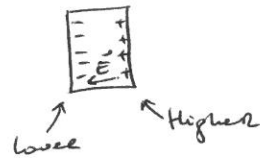
$$q < 0 \quad \vec{F}_B \div -\hat{x} \text{ direction}$$



- b.) What is the potential Difference?
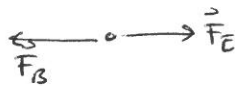
$$\vec{F}_E = q\vec{E} \quad (q < 0 \rightarrow \vec{F}_E : \text{rightwards})$$



Eventually: $F_B = F_E$

$$V = Ed$$

$$F_E = |q|E$$

$$F_B = |q|vB \sin \phi \leftarrow 90^\circ$$

$$F_E = F_B$$

$$|q|E = |q|vB$$

$$E = vB$$

$$V = Ed = vBd (= 3 \text{ mV})$$